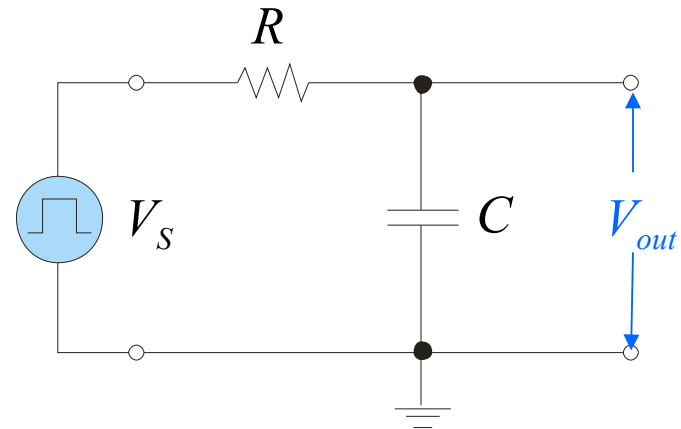


# The RC Integrator

An  $RC$  integrator is a circuit that approximates the mathematical process of integration. Integration is a summing process, and a basic integrator can produce an output that is a running sum of the input under certain conditions.


A basic  $RC$  integrator circuit is simply a capacitor in series with a resistor and the source. The output is taken across the capacitor.


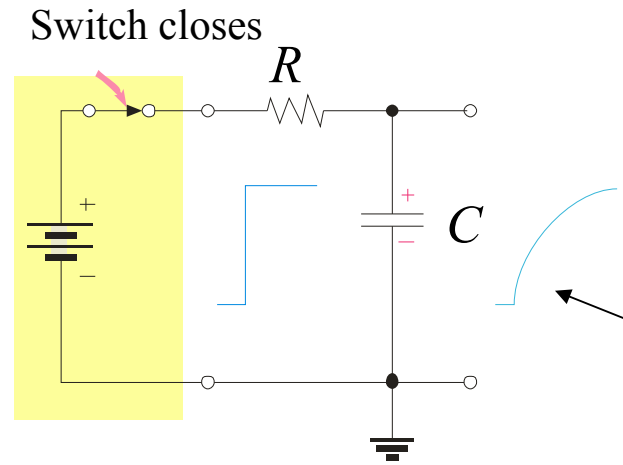
# The RC Integrator

When a pulse generator is connected to the input of an  $RC$  integrator, the capacitor will charge and discharge in response to the pulses.

When the input pulse goes HIGH, the pulse generator acts like a battery in series with a switch and the capacitor charges.




The output is an exponentially rising curve.
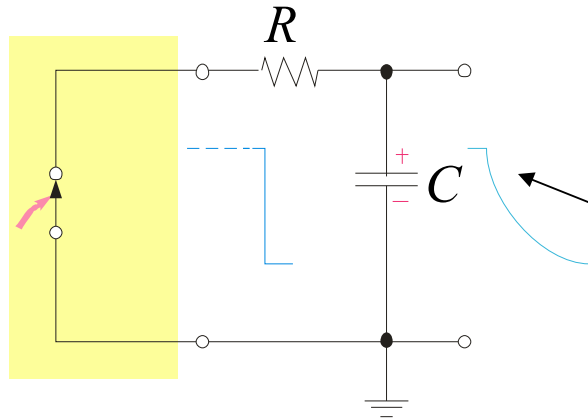
# The RC Integrator


When the pulse generator goes low, the small internal impedance of the generator makes it look like a closed switch has replaced the battery.

The pulse generator now acts like a closed switch and the capacitor discharges.




The output is an exponentially falling curve.

# Examples

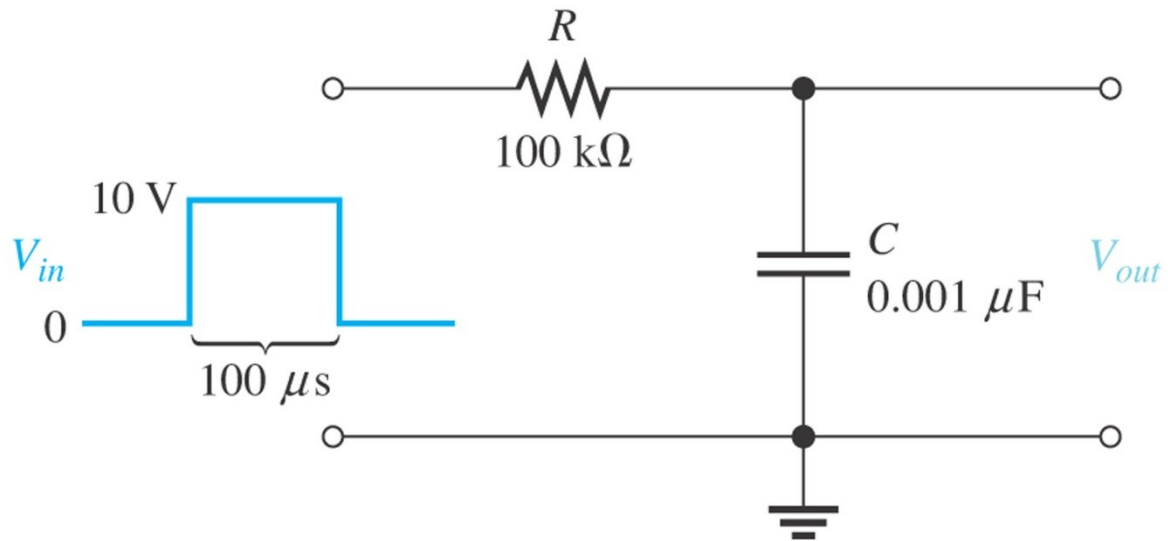


# Solution

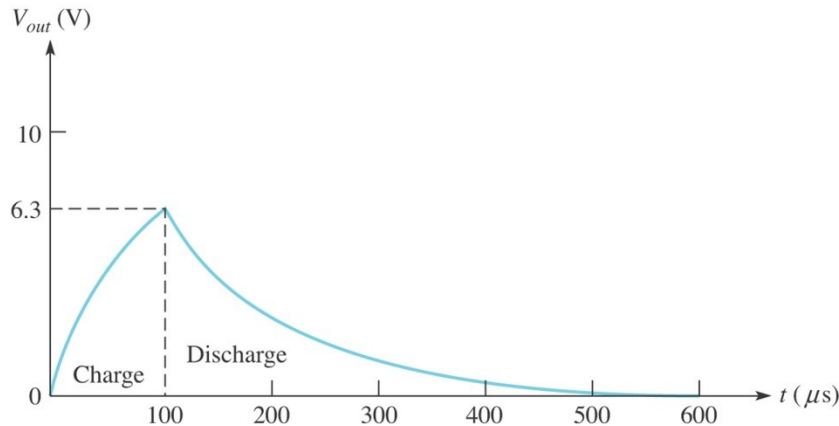1. Time constant  $\tau = RC = (100K\Omega)(0.001\mu F) = 100\mu s$
2. Compute the  $V_{out}$  for one time constant  
$$V_{out} = (0.63)10V = 6.3V$$
3. Time to finish discharging  $5\tau = 500\mu s$


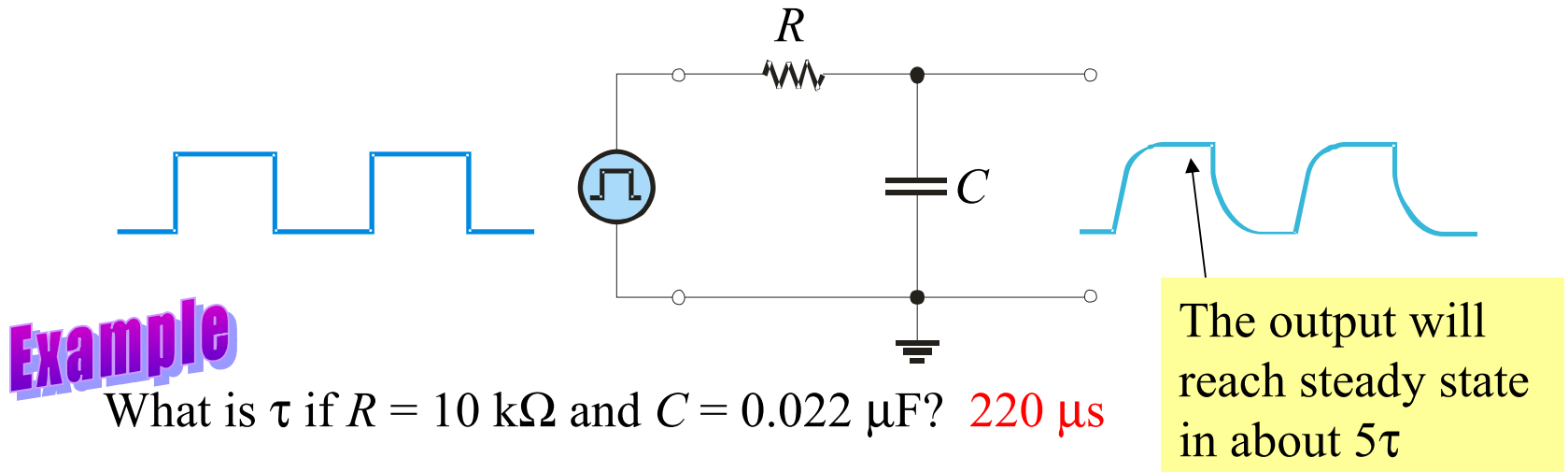
# The RC Integrator


Waveforms for the  $RC$  integrator depend on the time constant ( $\tau$ ) of the circuit. If the time constant is short compared to the period of the input pulses, the capacitor will fully charge and discharge. For an  $RC$  circuit,  $\tau = RC$ . The output will reach 63% of the final value in  $1\tau$ .



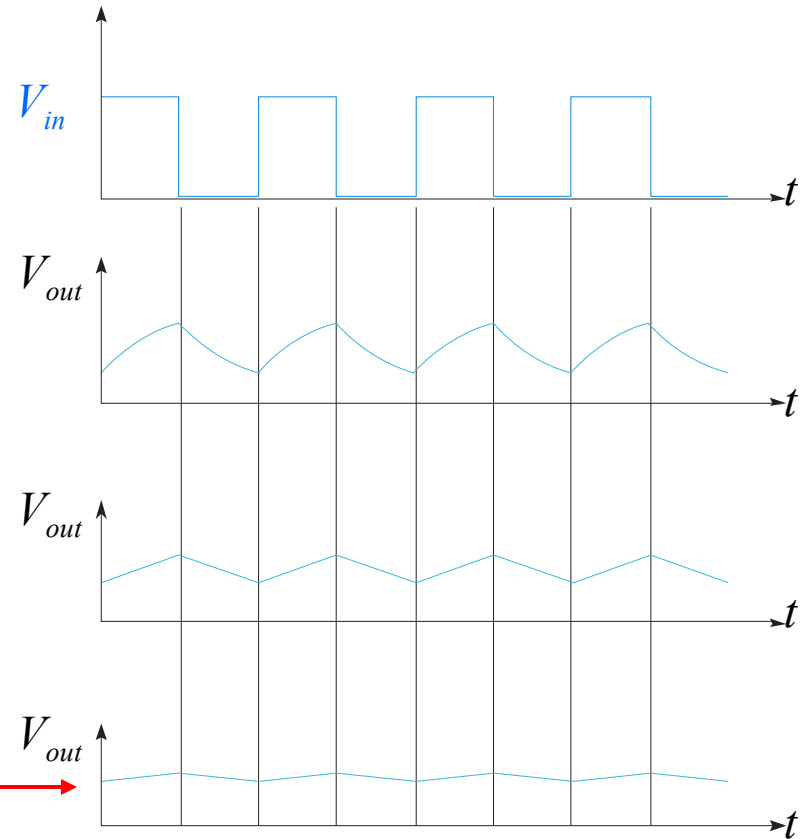
# The RC Integrator

If  $\tau$  is increased, the waveforms approach the average dc level as in the last waveform. The output will appear triangular but with a smaller amplitude.

Alternatively, the input frequency can be increased ( $T$  shorter). The waveforms will again approach the average dc level of the input.



# Example

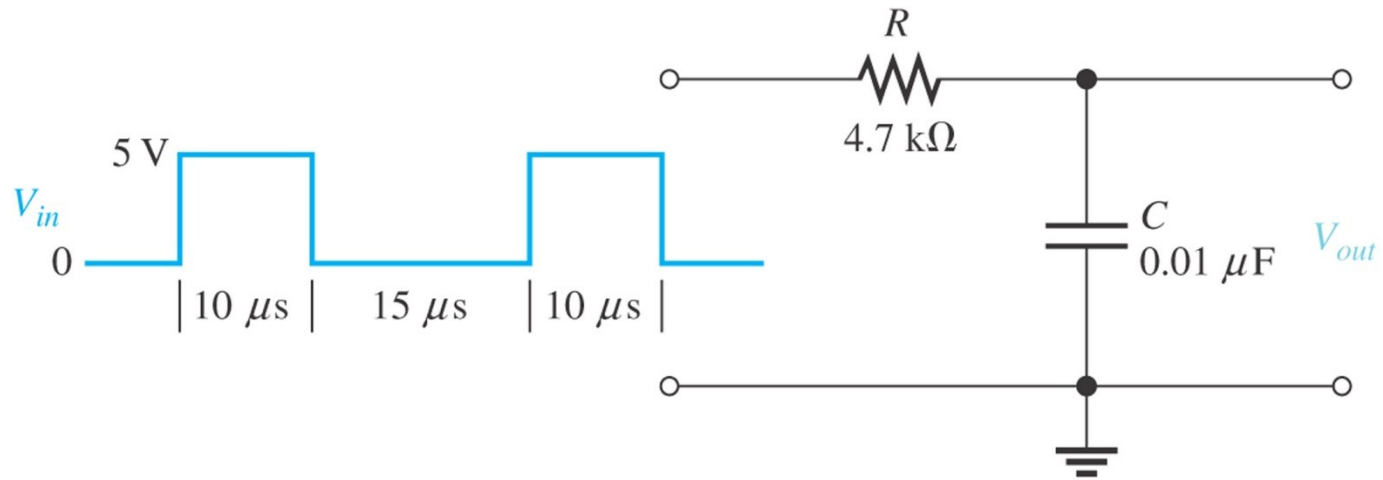



# Solution

1. Time constant  $\tau = RC = (4.7K\Omega)(0.01\mu F) = 47\mu s$

2. Calculate the first pulse

$$V_C = V_F (1 - e^{-\frac{t}{\tau}}) = 5(1 - e^{-\frac{10}{47}}) = 958mv$$



3. Calculate the second pulse

$$V_C = V_i (e^{-\frac{t}{\tau}}) = 958(e^{-\frac{15}{47}}) = 696mv$$

4. Calculate the second pulse

$$V_C = V_F + (V_i - V_F)e^{-\frac{t}{\tau}} = 5 + (696mV - 5V)e^{-\frac{10}{47}} = 1.52V$$


# Solution

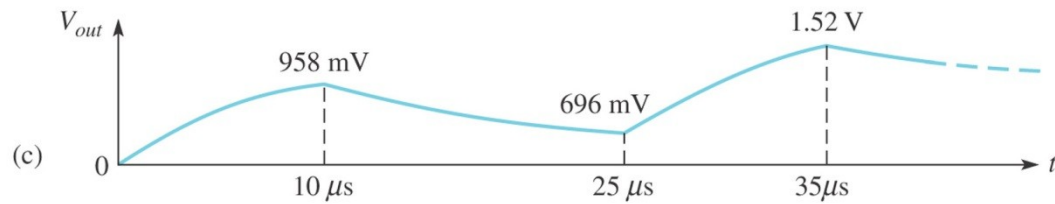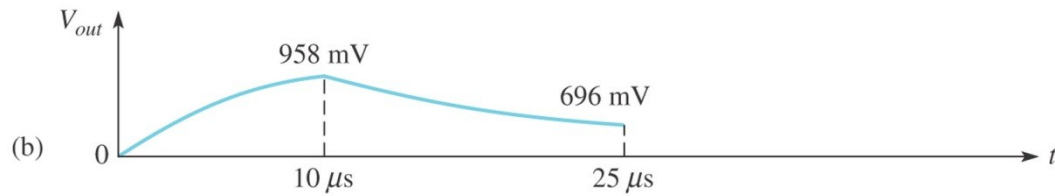
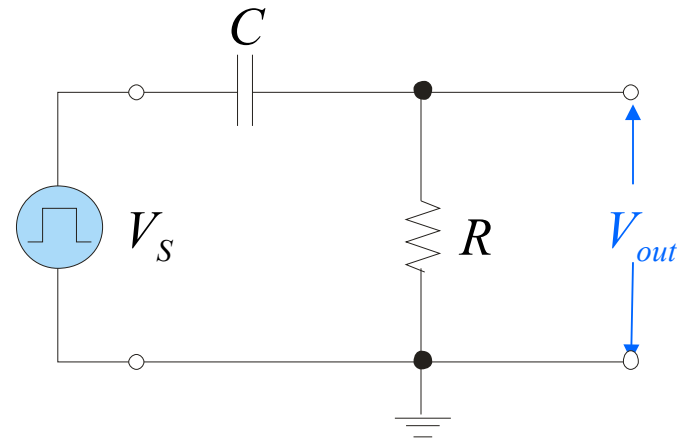
# The RC Differentiator

An  $RC$  differentiator is a circuit that approximates the mathematical process of differentiation. Differentiation is a process that finds the rate of change, and a basic differentiator can produce an output that is the rate of change of the input under certain conditions.


A basic  $RC$  differentiator circuit is simply a resistor in series with a capacitor and the source. The output is taken across the resistor.


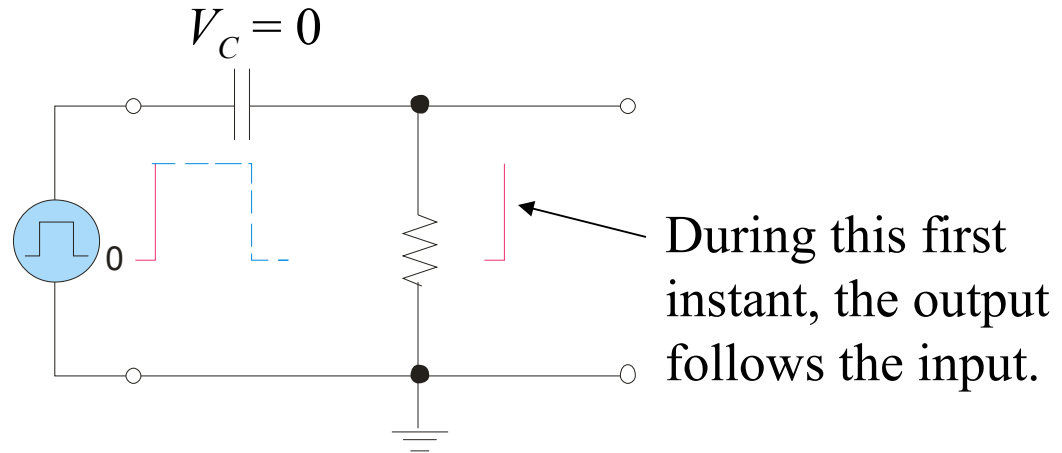
# The RC Differentiator

When a pulse generator is connected to the input of an  $RC$  differentiator, the capacitor appears as an instantaneous short to the rising edge and passes it to the resistor.


The capacitor looks like a short to the rising edge because voltage across  $C$  cannot change instantaneously.


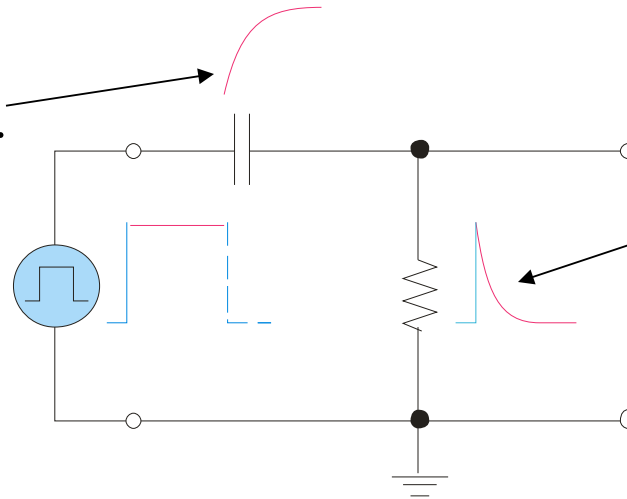
# The RC Differentiator


After the initial edge has passed, the capacitor charges and the output voltage decreases exponentially.

The voltage across  $C$  is the traditional charging waveform.




The output decreases as the pulse levels off.

# Example

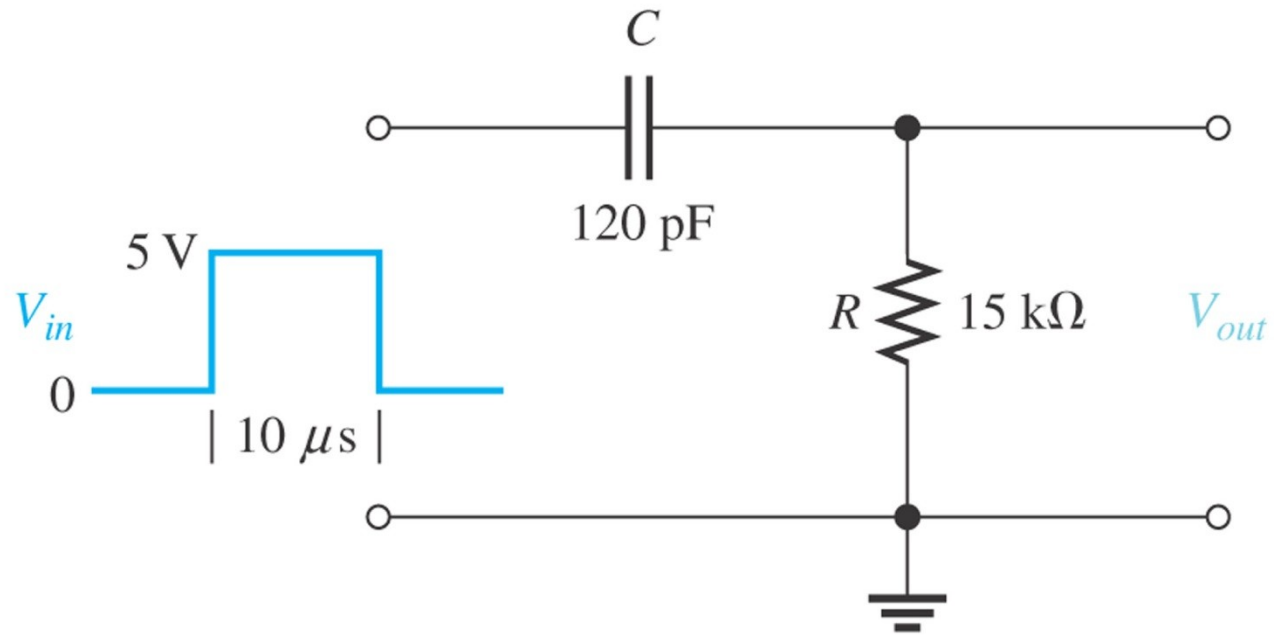

# Solution

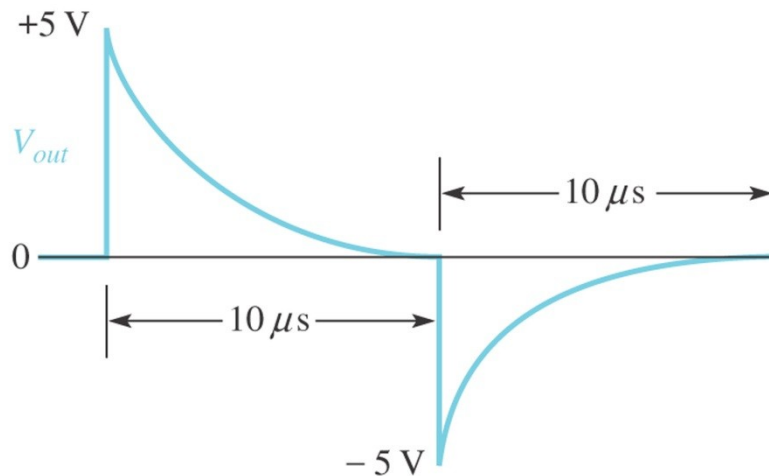
1. Time constant  $\tau = RC = (15K\Omega)(120\mu F) = 1.8\mu s$
2. tw is bigger than 5 time constant 90 us


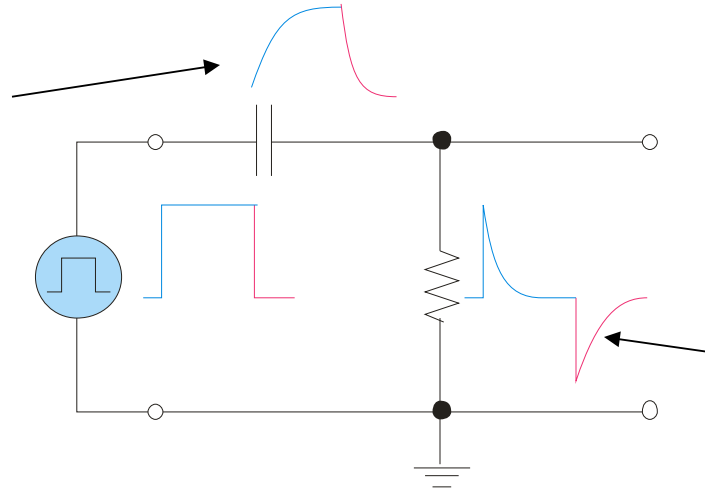
# The RC Differentiator

The falling edge is a rapid change, so it is passed to the output because the capacitor voltage cannot change instantaneously. The type of response shown happens when  $\tau$  is much less than the pulse width ( $\tau \ll t_w$ ).

The voltage across  $C$  when the input goes low decreases exponentially.




After dropping to a negative value, the output voltage increases exponentially as the capacitor discharges.


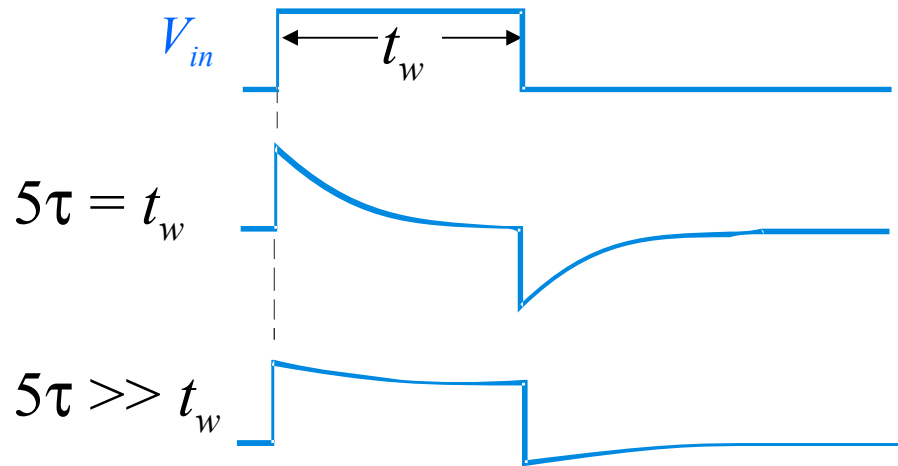
# The RC Differentiator

The output shape is dependent on the ratio of  $\tau$  to  $t_w$ .

When  $5\tau = t_w$ , the pulse has just returned to the baseline when it repeats.



If  $\tau$  is long compared to the pulse width, the output does not have time to return to the original baseline before the pulse ends. The resulting output looks like a pulse with “droop”.


# The RL Integrator

Like the  $RC$  integrator, an  $RL$  integrator is a circuit that approximates the mathematical process of integration. Under equivalent conditions, the waveforms look like the  $RC$  integrator. For an  $RL$  circuit,  $\tau = L/R$ .


A basic  $RL$  integrator circuit is a resistor in series with an inductor and the source. The output is taken across the resistor.
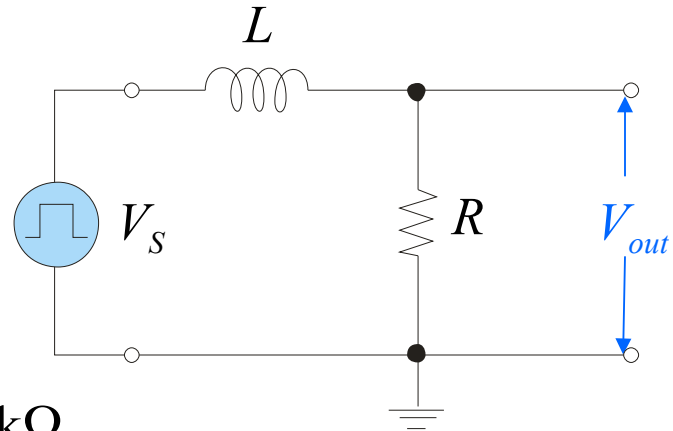
## Example

What is the time constant if  $R = 22 \text{ k}\Omega$  and  $L = 22 \text{ }\mu\text{H}$ ? **1.0 ms**




# Example

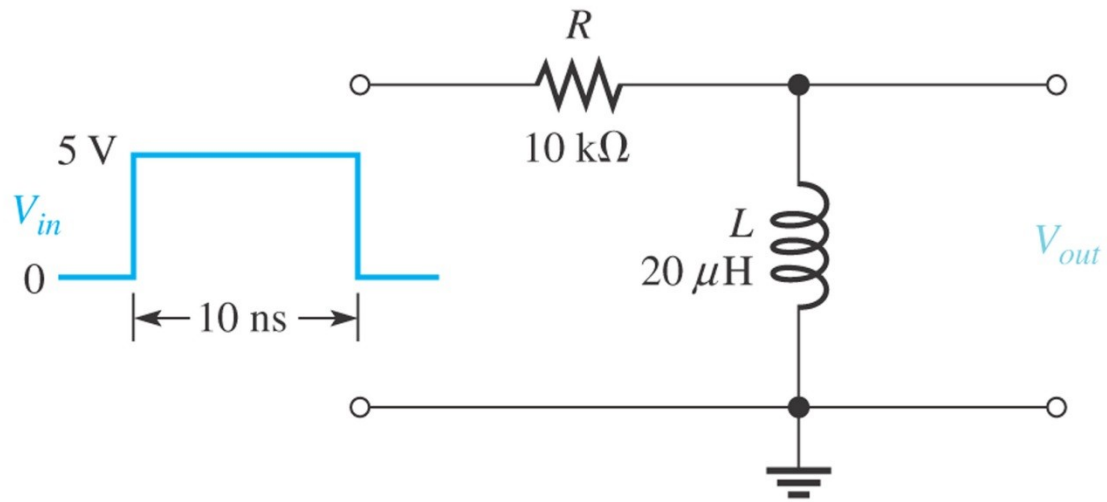

# Solution
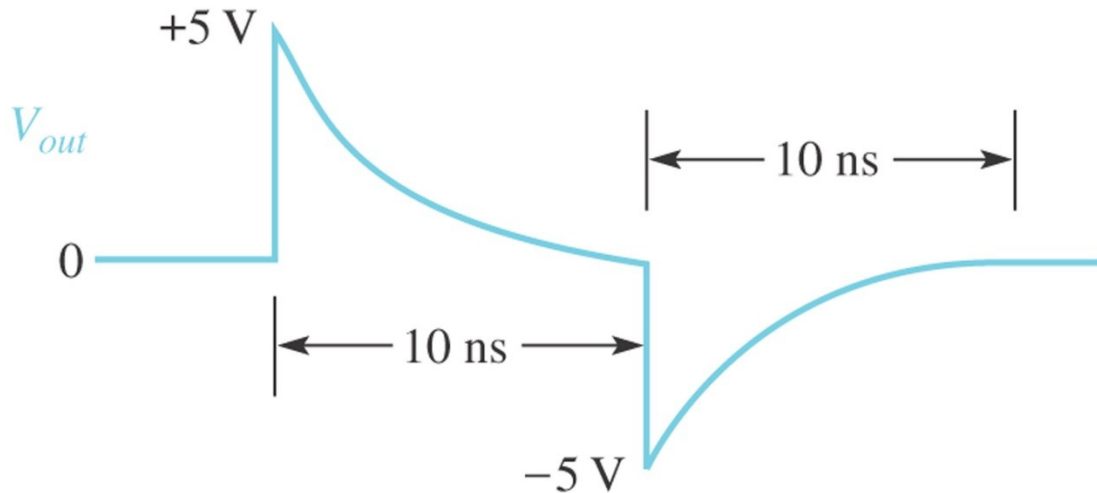
## 1. Time constant


$$\tau = \frac{L}{R} = \frac{20\mu H}{10k\Omega} = 2ns$$


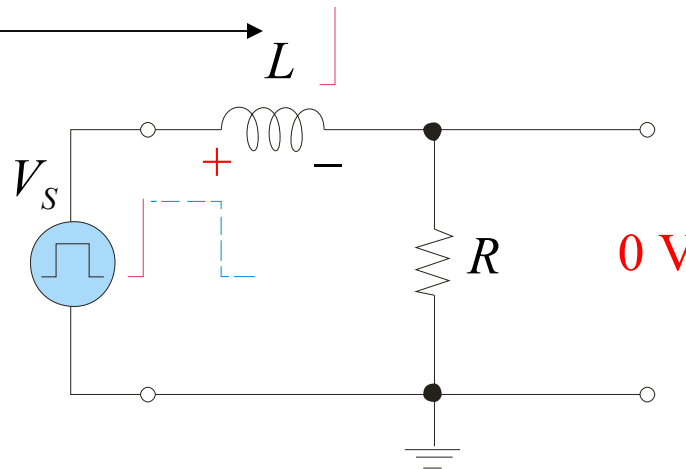
# The RL Integrator

When the pulse generator output goes high, a voltage immediately appears across the inductor in accordance with Lenz's law. The instantaneous current is zero, so the resistor voltage is initially zero.

The induced voltage across  $L$  opposes the initial rise of the pulse.




The output is initially zero because there is no current.
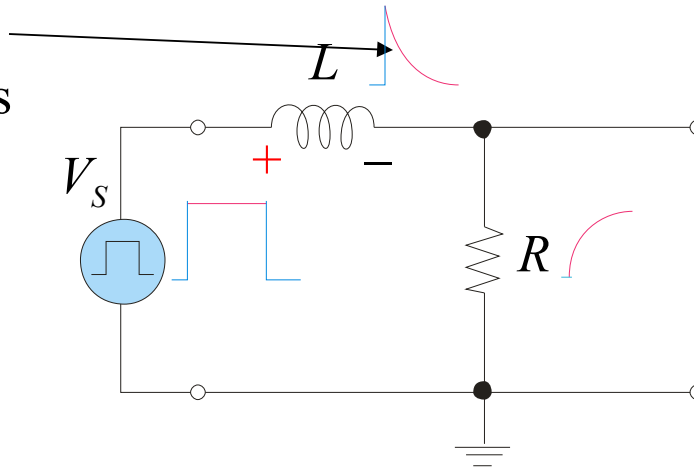
# The RL Integrator

At the top of the input pulse, the inductor voltage decreases exponentially and current increases. As a result, the voltage across the resistor increases exponentially. As in the case of the  $RC$  integrator, the output will be 63% of the final value in  $1\tau$ .

The induced voltage across  $L$  decreases.




The output voltage increases as current builds in the circuit.
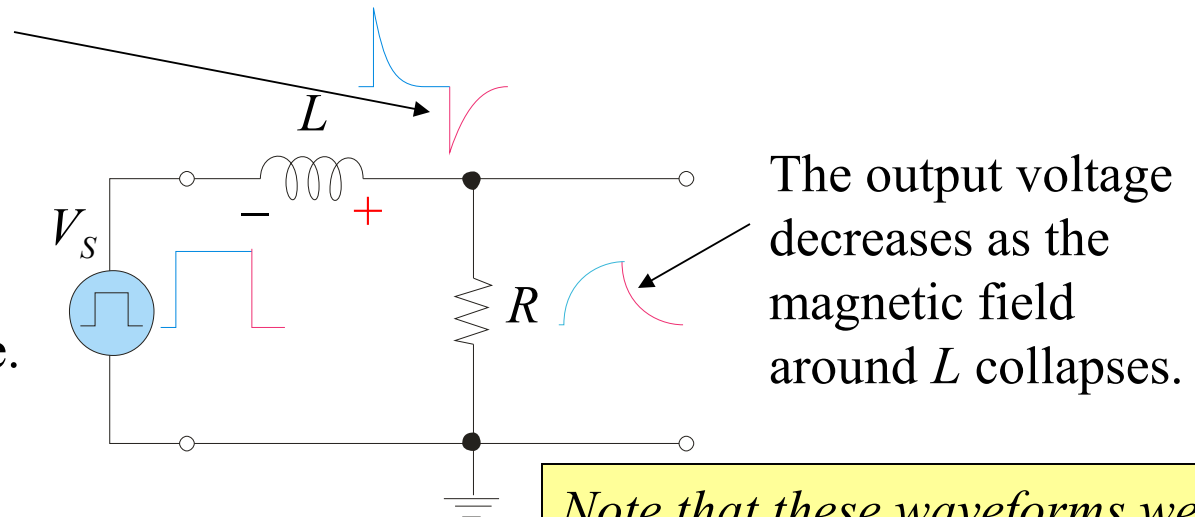
# The RL Integrator

When the pulse goes low, a reverse voltage is induced across  $L$  opposing the change. The inductor voltage initially is a negative voltage that is equal and opposite to the generator; then it exponentially increases.

The induced voltage across  $L$  initially opposes the change in the source voltage.




*Note that these waveforms were the same in the RC integrator.*
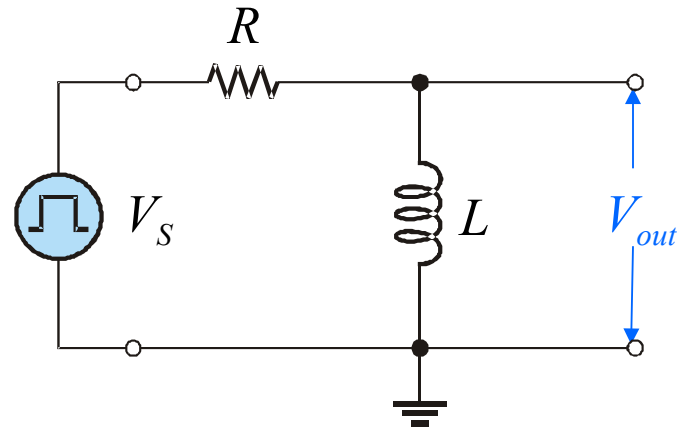
# The RL Differentiator

An  $RL$  differentiator is also a circuit that approximates the mathematical process of differentiation. It can produce an output that is the rate of change of the input under certain conditions.


A basic  $RL$  differentiator circuit is an inductor in series with a resistor and the source. The output is taken across the inductor.




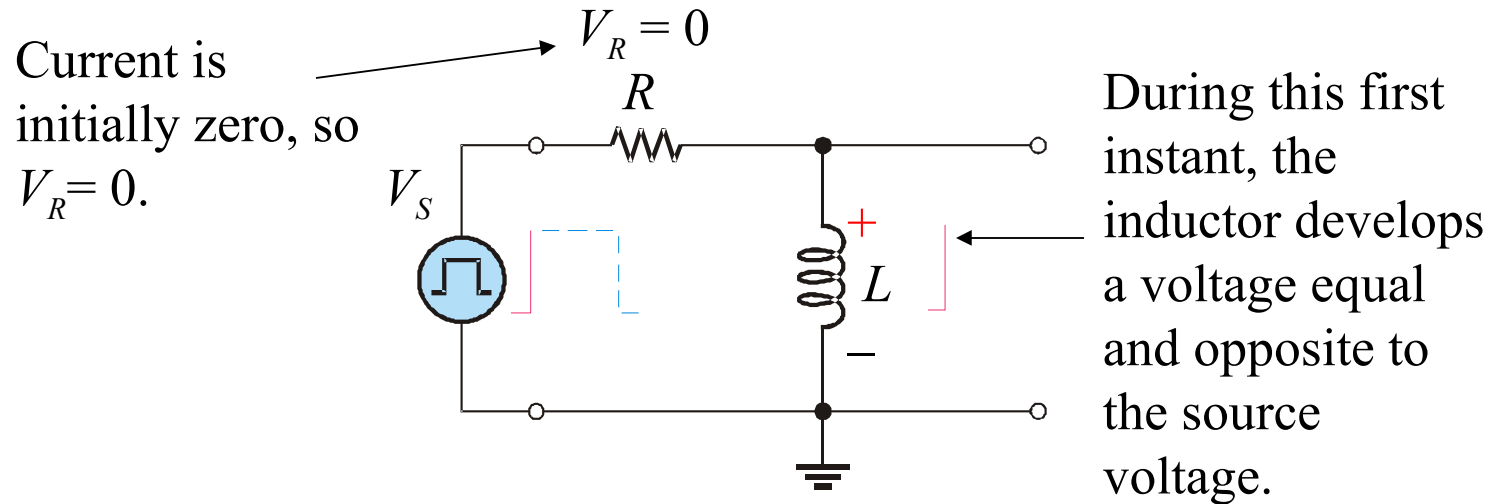
# The RL Differentiator


When a pulse generator is connected to the input of an  $RL$  differentiator, the inductor has a voltage induced across it that opposes the source; initially, no current is in the circuit.


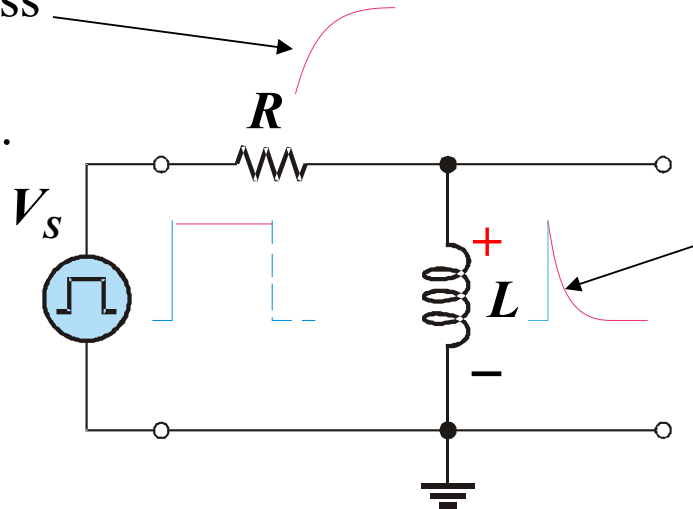
# The RL Differentiator

After the initial edge has passed, current increases in the circuit. Eventually, the current reaches a steady state value given by Ohm's law.

The voltage across  $R$  increases as current increases.




The output decreases as the pulse levels off.
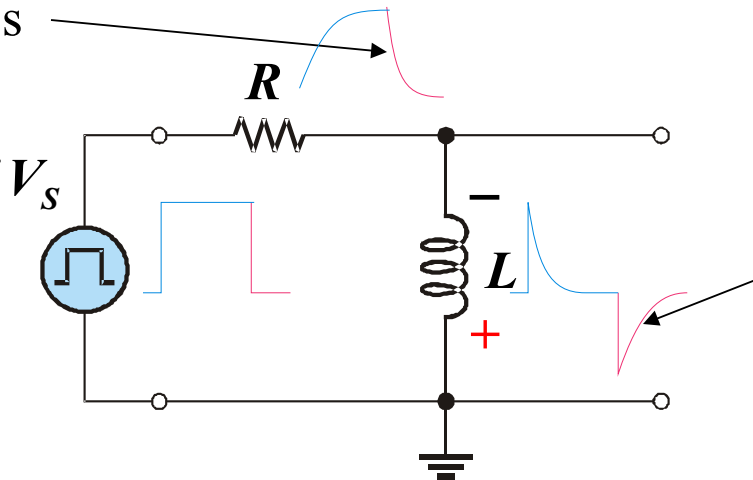
# The RL Differentiator

Next, the falling edge of the pulse causes a (negative) voltage to be induced across the inductor that opposes the change. The current decreases as the magnetic field collapses.

The voltage across  $R$  decreases as current decreases.




The output decreases initially and then increases exponentially.

# The RL Differentiator

As in the case of the *RC* differentiator, the output shape is dependent on the ratio of  $\tau$  to  $t_w$ .

When  $5\tau = t_w$ , the pulse has just returned to the baseline when it repeats.

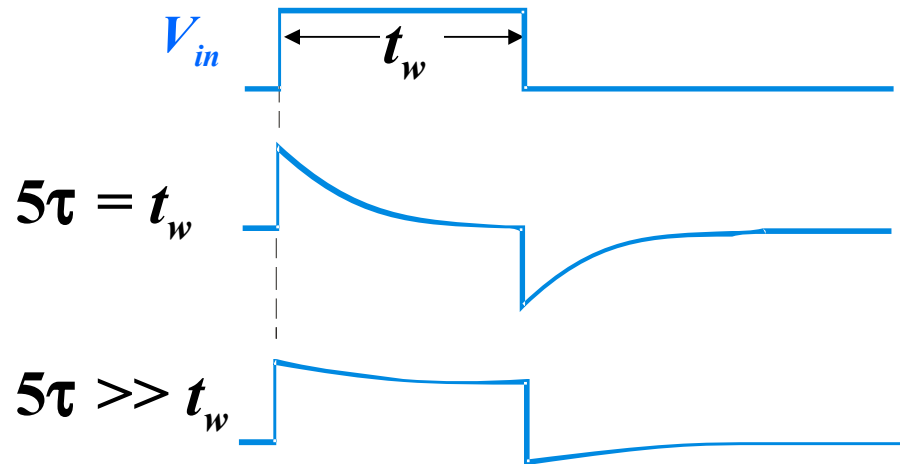If  $\tau$  is long compared to the pulse width, the output looks like a pulse with “droop”.



# Application

An application of an integrator is to generate a time delay. The voltage at  $B$  rises as the capacitor charges until the threshold circuit detects that the capacitor has reached a predetermined level.

